



Trinity College Dublin
Coláiste na Tríonóide, Baile Átha Cliath
The University of Dublin

3C7 Assignment 2

Clovis Hanbury-Tenison

20331969

3C7 ASSIGNMENT 2

Student Name:	Clovis Hanbury-Tenison
Student ID Number:	20331969
Assessment Title:	Assignment 2
Lecturer (s):	SHREEJITH SHANKER
Date Submitted	14/04/2023

I hereby declare that this assessment submission is entirely my own work and that it has not been submitted as an exercise for a degree at this or any other university.

I hereby declare that I have not shared any part of this submission with any other student or person.

I have read and I understand the plagiarism provisions in the General Regulations of the University Calendar for the current year, found at: <http://www.tcd.ie/calendar>

I have also completed the Online Tutorial on avoiding plagiarism 'Ready, Steady, Write', located at <http://tcd-ie.libguides.com/plagiarism/ready-steady-write>

I am aware that the module coordinator reserves the right to submit my exam to Turnitin and may follow up with further actions if required should I be found to have breached College policy on plagiarism

Signed:



Date:

14/04/2023

ABSTRACT

For Assignment 2 we were to implement a FSM, finite state machine to our LFSR from Lab F. A Moore counter was to be implemented in our FSM so that we could check for iterations of the binary pattern 10011110011. Our LFSR consisted of 17 total bits. The first bit was the feedback bit which was an XOR output of our 17th and 14th bit, as instructed in the Xilinx documentation.

As the pattern we were looking for was 11 bits and our LFSR consisted of 17 bits. We used 6 Moore counter machines to count all the iterations through the LFSR. Our Moore counter machine consisted of 11 states, corresponding to each bit of our pattern. Each state has two next states which would be called depending on our input bit. This meant we would be able to minimize the operation by not returning to state0 every time the next bit was unideal for our pattern.

The pattern counter was reset every LFSR cycle as our aim was to count the number of patterns in one cycle. The FSM was then implemented onto our Basys board along with our LFSR, and the count was displayed on our seven segment display and count of our pattern in our LFSR was found to be 312 appearances.

INTRODUCTION

A Moore counter Finite State Machine was create for Assignment 2. An FSM is a system that is able to simulate sequential logic. The FSM we create had 11 states, and each had two next states which can be seen in the diagram below. The FSM was created to find a pattern in our LFSR. This was then counted so that we could display the amount of times the pattern appeared in one cycle of our LFSR. I n a practical implementation of an FSM, an operation could happen whenever this pattern is detected.

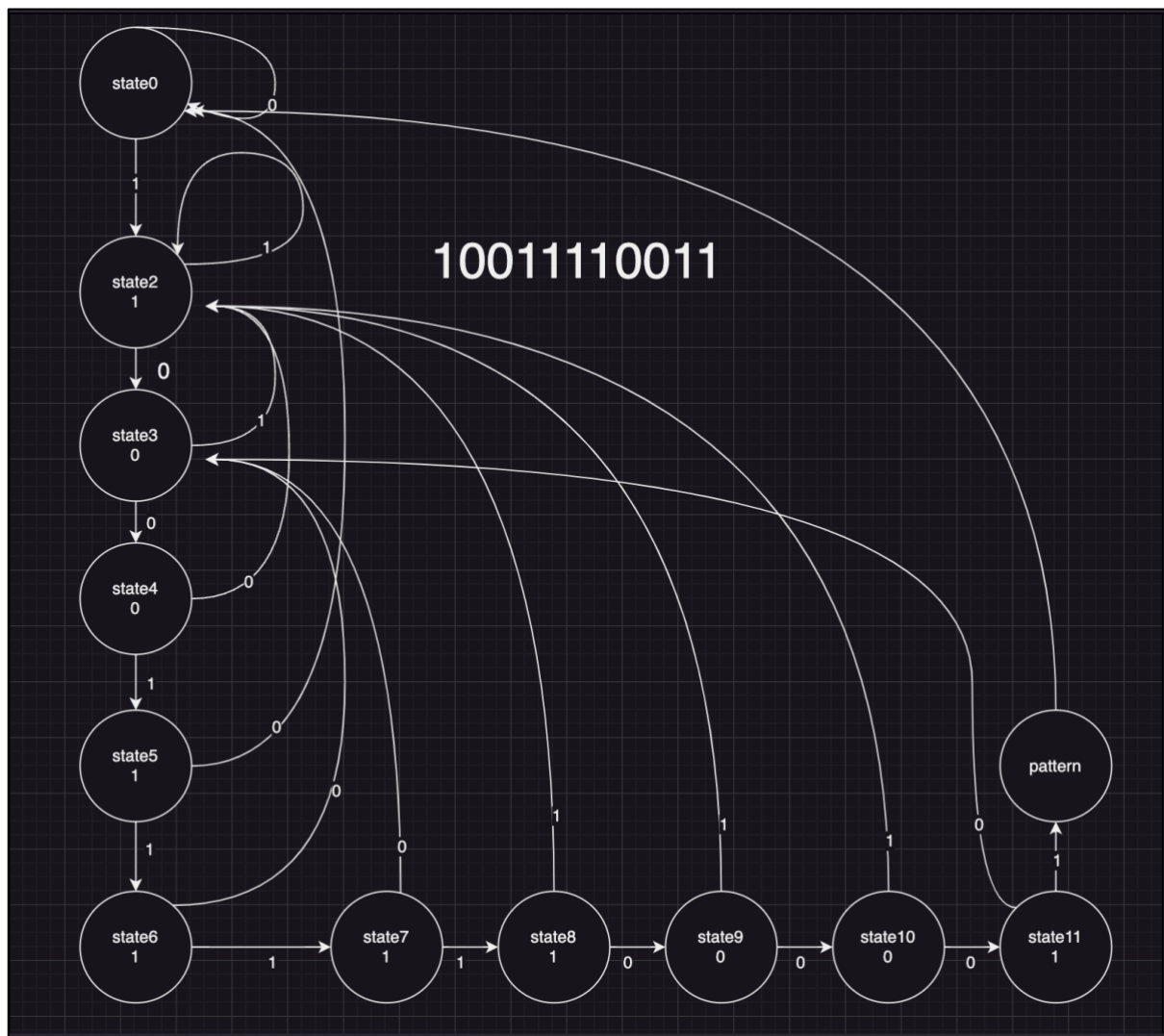


Figure 0 (FSM sequential states)

BODY

For our Top Module, we used our LFSR submodule and we used our 6 Moore Machines modules which took in bits 0, 1, 2, 3, 4, 5 of our LFSR so that we could account for all of our pattern appearances. We also implemented the seven segment display submodule and the CLK module, so that we would be able to run the programme at our desired speed using the Basys boards Clock and display our pattern count on the seven segment of the Basys board.

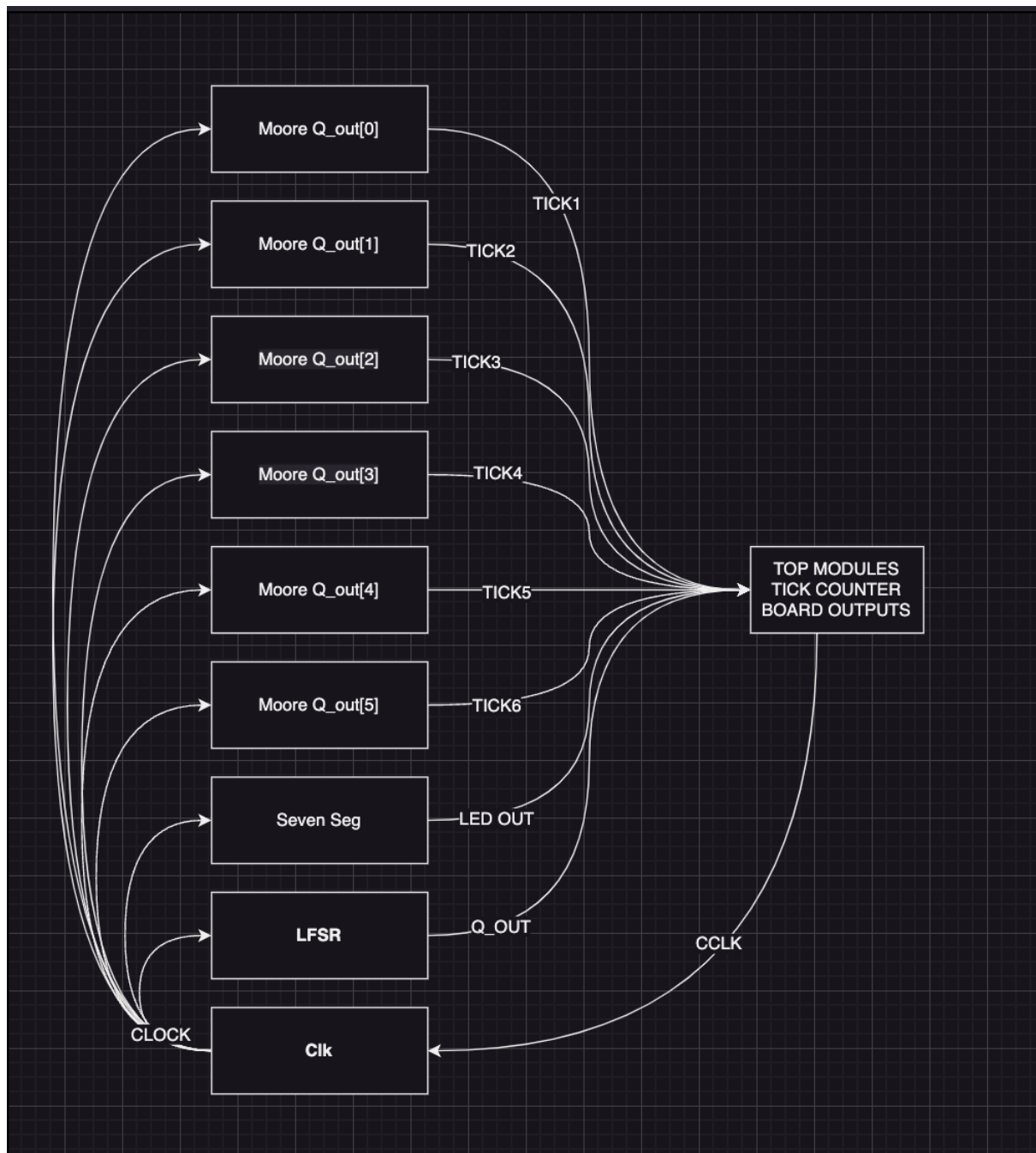


Figure 1.0 (Block Diagram of System)

Sources/Constraints/simulation Hierarchy

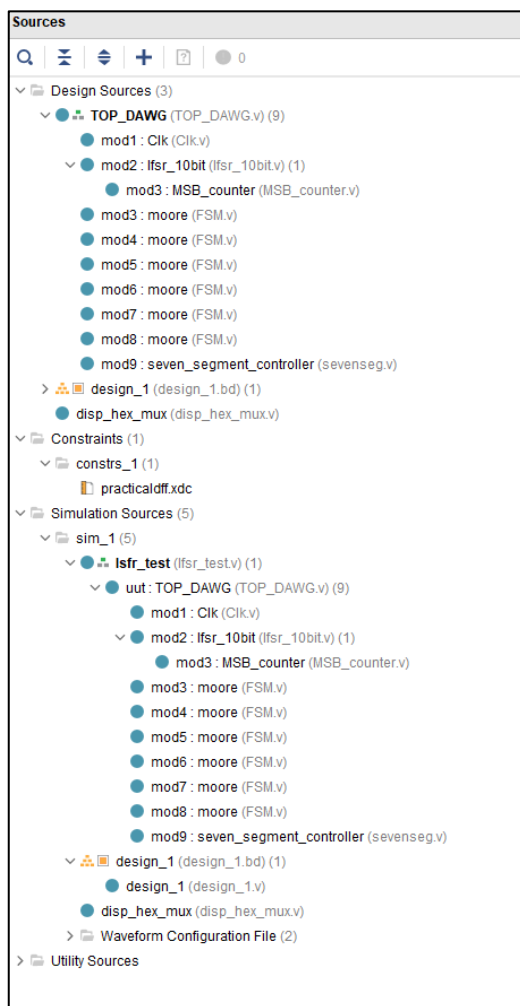


Figure 1.1 (List of modules, test case and constraints file hierarchy)

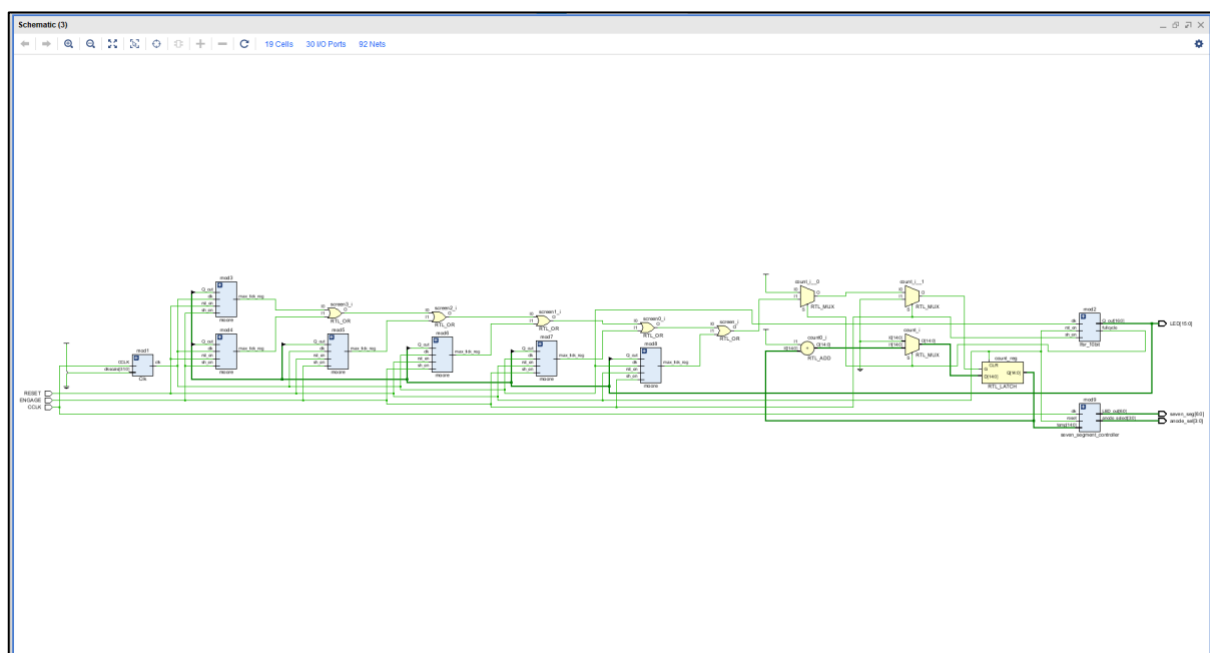


Figure 1.2 (Diagram of the complete system)

Our FSM was created using 11 states in an always block. Each state checked if the desired input LFSR bit matched with the next state and if so incremented to the next state and if not went back to the last state which would keep the pattern sequence going. This was done for each of the 11 states and in the last case, if the pattern was found, a max_tick_reg was set to high while also restating the state back to the 1st.

 


Figure 1.3 (Schematic of the FSM /Moore Machines)

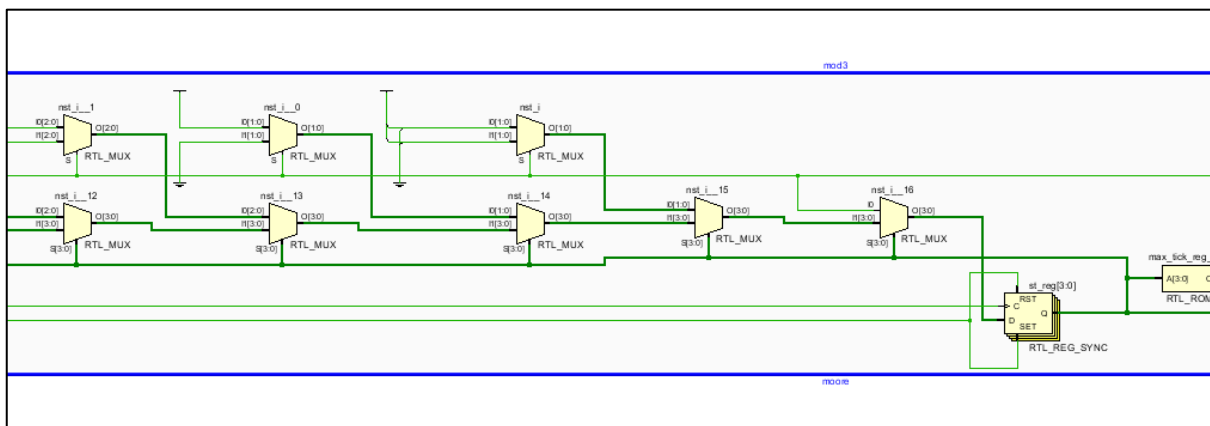


Figure 1.4 (ZOOM of Schematic of the FSM /Moore Machines)

The pattern tick outputs of each of our Moore counter machines s1, s2, s3, s4, s5 and s6 were def through OR logic so that we could assign them to a single wire called screen, we then used this to increment our counter. This was done in our top module, extra conditions to reset the count back to 0 were set for reset and when our LFSR cycle was over.

The seven segment display was taken from the provide code in Lab F and altered slightly, with each display configured to display the value using remainders and division, as Verilog and binary do not accept decimals, this would automatically take our value and reduce it to the desired number as can be seen in the module file.

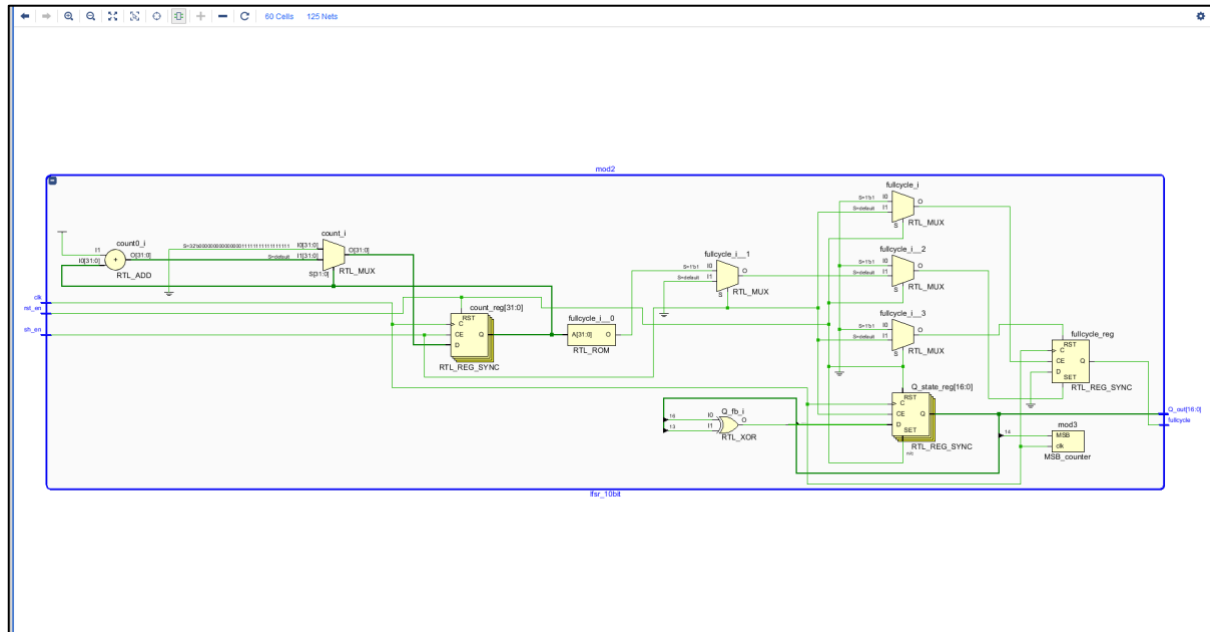


Figure 1.5 (ZOOM of Schematic of the LFSR)

The test was ran and the waveforms were found for our output, clock, tick and counter. We ran the test bench initially just taking the 1st bit of the LFSR into a Moore Machine and then tested again when we had implemented multiple Moore machines for each of the first six bits. Once the desired waveforms were found and we confirmed that our FSMs and counter was working correctly, we created a constraints file. The constraints file mapped 16 of our 17 bits to the boards LED's as we could not fit all 17. The V17 switch was set to ENGAGE and the V16 set to RESET, allowing us to halt and reset our LFSR. The Seven segment constraints were then added similarly to the constraints for seven segment provided in LAB F.

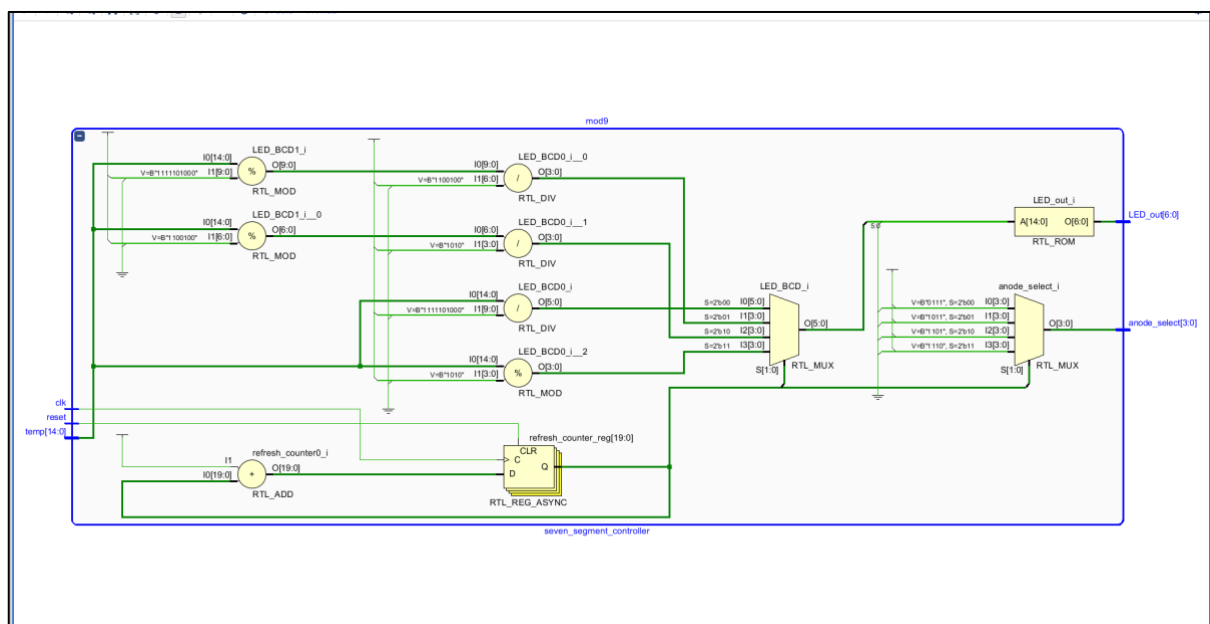


Figure 1.6 (Schematic of seven segment display module)

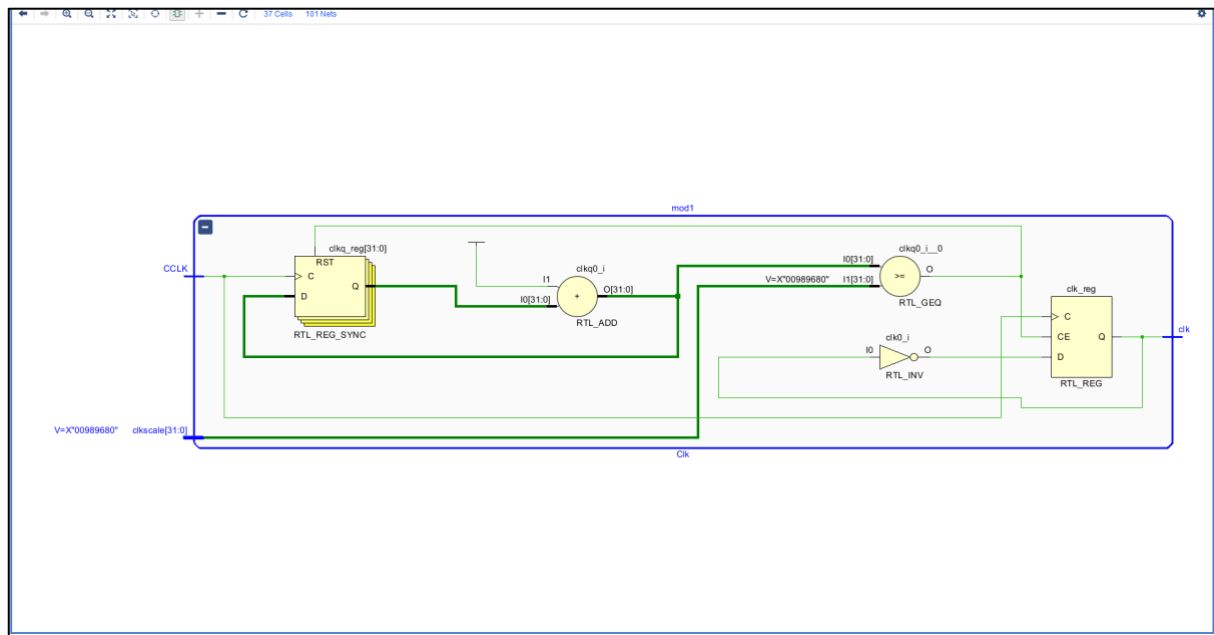


Figure 1.7 (Schematic of seven clock module)

This allowed us to generate a bitstream file and program the Basys board with our code. The board was tested using the RESET and ENGAGE switches. The shifting and counter were confirmed using our test cases and all the desired functions were confirmed such as resetting on RESET and once a full LFSR cycle had been completed. A video was taken to show our implementation working. As we wanted to demonstrate that all our functions worked, we sped up the clock speed so that the LFSR cycle wouldn't take too long.

 


Figure 1.9 (IO view of pin assignments)

```

## Clock signal
set_property PACKAGE_PIN W5 [get_ports CCLK]
set_property IOSTANDARD LVCMOS33 [get_ports CCLK]

set_property PACKAGE_PIN U16 [get_ports {LED[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[3]}]
set_property PACKAGE_PIN E19 [get_ports {LED[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[4]}]
set_property PACKAGE_PIN U19 [get_ports {LED[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[5]}]
set_property PACKAGE_PIN V19 [get_ports {LED[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[6]}]
set_property PACKAGE_PIN W18 [get_ports {LED[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[7]}]
set_property PACKAGE_PIN U15 [get_ports {LED[8]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[8]}]
set_property PACKAGE_PIN U14 [get_ports {LED[9]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[9]}]
set_property PACKAGE_PIN V14 [get_ports {LED[10]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[10]}]
set_property PACKAGE_PIN V13 [get_ports {LED[11]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[11]}]
set_property PACKAGE_PIN V3 [get_ports {LED[12]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[12]}]
set_property PACKAGE_PIN W3 [get_ports {LED[13]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[13]}]
set_property PACKAGE_PIN U3 [get_ports {LED[14]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[14]}]
set_property PACKAGE_PIN P3 [get_ports {LED[15]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[15]}]
set_property PACKAGE_PIN N3 [get_ports {LED[16]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LED[16]}]

set_property PACKAGE_PIN L1 [get_ports {screen}]
set_property IOSTANDARD LVCMOS33 [get_ports {screen}]

##Buttons

set_property PACKAGE_PIN V17 [get_ports {ENGAGE}]
set_property IOSTANDARD LVCMOS33 [get_ports {ENGAGE}]
set_property PACKAGE_PIN V16 [get_ports {RESET}]
set_property IOSTANDARD LVCMOS33 [get_ports {RESET}]

##7 segment display - Cathode pins
set_property PACKAGE_PIN W7 [get_ports {led_out[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[6]}]
set_property PACKAGE_PIN W6 [get_ports {led_out[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[5]}]
set_property PACKAGE_PIN U8 [get_ports {led_out[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[4]}]
set_property PACKAGE_PIN V8 [get_ports {led_out[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[3]}]
set_property PACKAGE_PIN U5 [get_ports {led_out[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[2]}]
set_property PACKAGE_PIN V5 [get_ports {led_out[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[1]}]
set_property PACKAGE_PIN U7 [get_ports {led_out[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {led_out[0]}]

#Anode Selects
set_property PACKAGE_PIN U2 [get_ports {anode_sel[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_sel[0]}]
set_property PACKAGE_PIN U4 [get_ports {anode_sel[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_sel[1]}]
set_property PACKAGE_PIN V4 [get_ports {anode_sel[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_sel[2]}]
set_property PACKAGE_PIN W4 [get_ports {anode_sel[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {anode_sel[3]}]

```

Figure 1.8 (constraints file for implementation)

All ports (30)												
anode_sel (4)	OUT					✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
anode_sel...	OUT			W4	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
anode_sel...	OUT			V4	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
anode_sel...	OUT			U4	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
anode_sel...	OUT			U2	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED (15)	OUT					(Multiple)	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[15]	OUT			L1	✓	✓	35	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[14]	OUT			P1	✓	✓	35	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[13]	OUT			N3	✓	✓	35	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[12]	OUT			P3	✓	✓	35	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[11]	OUT			U3	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[10]	OUT			W3	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[9]	OUT			V3	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[8]	OUT			V13	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[7]	OUT			V14	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[6]	OUT			U14	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[5]	OUT			U15	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[4]	OUT			W18	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[3]	OUT			V19	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[2]	OUT			U19	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[1]	OUT			E19	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
LED[0]	OUT			U16	✓	✓	14	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg (7)	OUT						34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			W7	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			W6	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			U8	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			V8	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			U5	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			V5	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
seven_seg...	OUT			U7	✓	✓	34	LVCMOS33*	+	3.300	12	✓ SLOW ✓ NONE ✓ PP_VTT_50 ✓
Scalar ports (3)												

Figure 1.10 (list view of pin assignments)

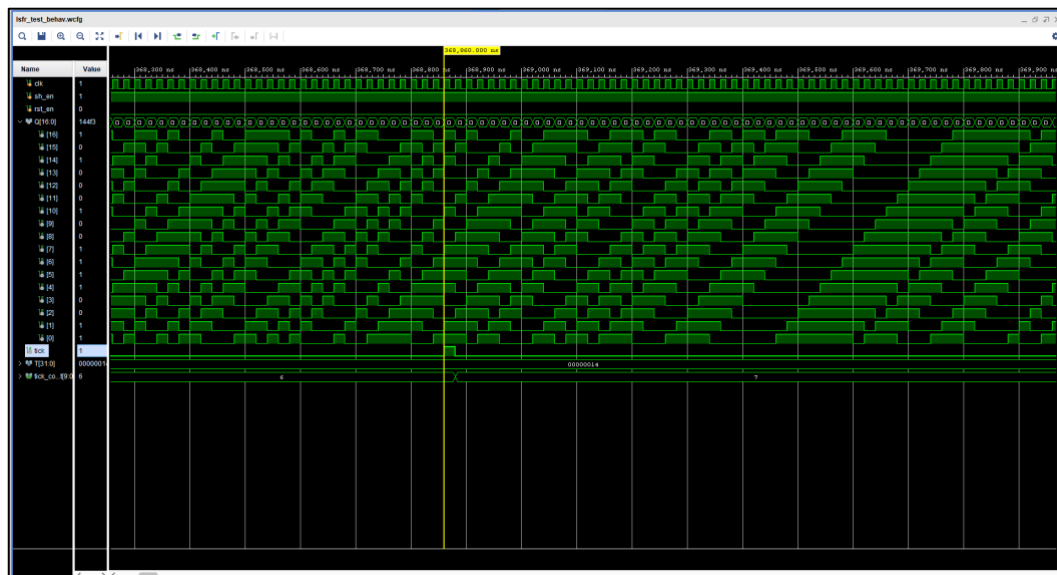


Figure 2.2 (Zoomed in implementation wave that shows the tick going high once and counter incrementing)

Our second and final test case was to check that the Top Module was working when we were implementing six Moore Machines. From here we tested initially, however we were unable to take six inputs to the same screen/tick wire in top module. So Logic had to be implemented to OR each tick, s1, s2, s3, s4, s5 and s6 from the Moore machines. This allowed us to display all the ticks and increment the counter for all.

As we can see in the zoomed in view. The counter increments six times when the tick is high. As the tick is staying in high state for six clock cycles. We are also able to see in our new wave forms that the counter is resetting when the LFSR cycle register goes high.

 


Figure 2.3 (Implementation Wave forms from Six Moore Machine system)

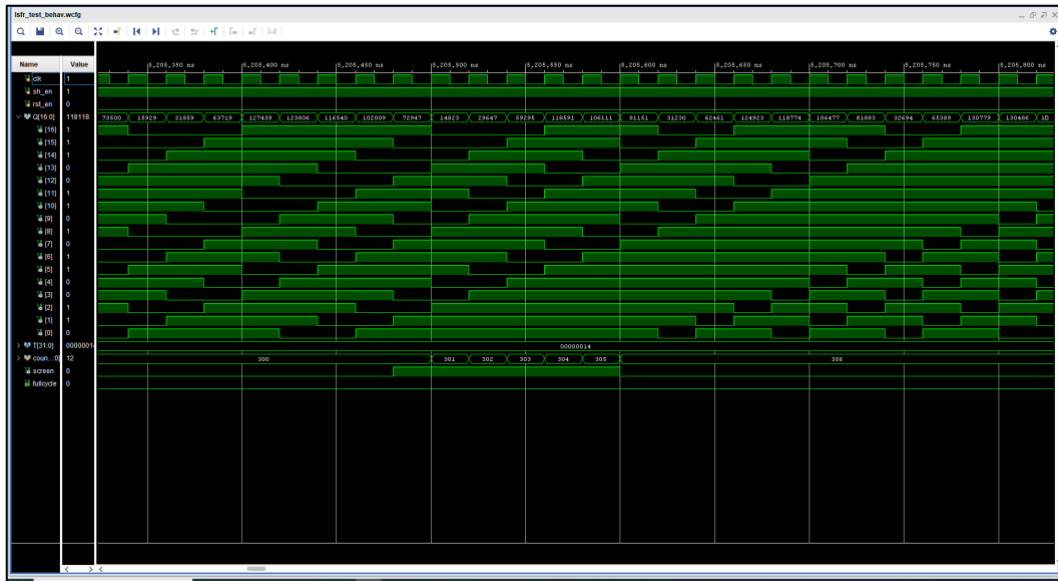


Figure 2.4 (Zoom of Implementation Wave forms from Six Moore Machine system showing six increments to previous one)

UTILIZATION REPORT/FLIP FLOP COUNT

The utilization report obtained from our implementation can be seen below. It gives the user an idea of how much of the board they are targeting and how much more operations the board could handle. As we can see we do not use very much of our Basys board and the board would be capable of much more, as would be expected of a board at this price.

In part 1 of the utilization report, we are provided with a number for the amount of flip flops that are in use in our system. In our system we use 158 of 41600 registers available on the Basys board as flip flops, coming to 0.38% of what we would be able to use if we were to want to. This number really gives us a good idea of how much can be done on a FPGA board and the huge possibility of complicated and large operations and systems that could be run.

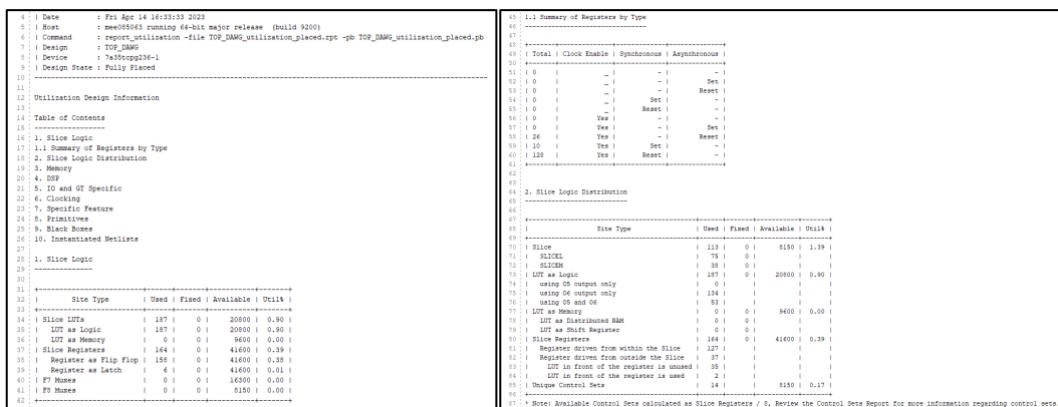


Figure 2.5 (Utilization report part1)

Figure 2.6 (Utilization report part2)

```

91: 3. Memory
92: -----
93: | Site Type | Used | Fixed | Available | Util% |
94: |-----|-----|-----|-----|-----|
95: | Block RAM Tile | 0 | 0 | 50 | 0.00 |
96: | RAMB16/FIFO* | 0 | 0 | 50 | 0.00 |
97: | RAMB16 | 0 | 0 | 100 | 0.00 |
98: |-----|-----|-----|-----|-----|
99: * Note: Each Block RAM Tile only has one FIFO logic available and therefore can accommodate only one FIFO16E1 or one FIFO16E1. However, if a FIFO16E1 occupies a Block RAM Tile, that tile can still accommodate a RAMB16E1
100:
101:
102: 4. DSP
103: -----
104: | Site Type | Used | Fixed | Available | Util% |
105: |-----|-----|-----|-----|-----|
106: | DSPs | 0 | 0 | 90 | 0.00 |
107: |-----|-----|-----|-----|-----|
108:
109: 5. IO and GT Specific
110: -----
111: | Site Type | Used | Fixed | Available | Util% |
112: |-----|-----|-----|-----|-----|
113: | Bonded IOB | 30 | 30 | 104 | 28.30 |
114: | IOB Master Pads | 14 | 1 | 1 | 1 |
115: | IOB Slave Pads | 15 | 1 | 1 | 1 |
116: | Bonded I/Os | 0 | 0 | 10 | 0.00 |
117: | Bonded OADs | 0 | 0 | 4 | 0.00 |
118: | PHY_CONFIG | 0 | 0 | 8 | 0.00 |
119: | FRAMER_REF | 0 | 0 | 5 | 0.00 |
120: | OUT_FIFO | 0 | 0 | 20 | 0.00 |
121: | IN_FIFO | 0 | 0 | 20 | 0.00 |
122: | IDELAYCTRL | 0 | 0 | 8 | 0.00 |
123: | INOVOS | 0 | 0 | 104 | 0.00 |
124: | GTXPS_CHANNEL | 0 | 0 | 2 | 0.00 |
125: | FRAMER_OUT/FRAMER_OUT_PHY | 0 | 0 | 20 | 0.00 |
126: | FRAMER_IN/FRAMER_IN_PHY | 0 | 0 | 20 | 0.00 |
127: | IDELAY2/IDELAY2_FINDELAY | 0 | 0 | 250 | 0.00 |
128: | INOVOS_GATE | 0 | 0 | 2 | 0.00 |
129: | ILOGIC | 0 | 0 | 106 | 0.00 |
130: | OLOGIC | 0 | 0 | 106 | 0.00 |
131: |-----|-----|-----|-----|-----|
132:

```

Figure 2.7 (Utilization report part3)

```

174: 8. Primitives
175: -----
176: | Ref Name | Used | Functional Category |
177: |-----|-----|-----|
178: | FDSR | 128 | Flop & Latch |
179: | LUT2 | 64 | LUT |
180: | LUT5 | 58 | LUT |
181: | CARRY4 | 57 | CarryLogic |
182: | LUT4 | 49 | LUT |
183: | LUT6 | 41 | LUT |
184: | OSUF | 27 | IO |
185: | FDSR | 20 | Flop & Latch |
186: | LUT3 | 18 | LUT |
187: | LUT1 | 10 | LUT |
188: | FDSR | 10 | Flop & Latch |
189: | LDCR | 6 | Flop & Latch |
190: | ISUF | 3 | IO |
191: | BUF8 | 2 | Clock |
192: |-----|-----|-----|
193:
194: 9. Black Boxes
195: -----
196: | Ref Name | Used |
197: |-----|-----|
198:
199:
200: 10. Instantiated Netlists
201: -----
202: | Ref Name | Used |
203: |-----|-----|
204:
205:
206:
207:
208:
209:
210:
211:
212:
213: 6. Clocking
214: -----
215: | Site Type | Used | Fixed | Available | Util% |
216: |-----|-----|-----|-----|-----|
217: | BUFCTRL | 2 | 0 | 32 | 6.25 |
218: | BUFIO | 0 | 0 | 20 | 0.00 |
219: | MMCM2_ADV | 0 | 0 | 5 | 0.00 |
220: | PLL2_ADV | 0 | 0 | 5 | 0.00 |
221: | BUFMRCE | 0 | 0 | 10 | 0.00 |
222: | BUFHCE | 0 | 0 | 72 | 0.00 |
223: | BUFR | 0 | 0 | 20 | 0.00 |
224: |-----|-----|-----|-----|-----|
225:
226: 7. Specific Feature
227: -----
228: | Site Type | Used | Fixed | Available | Util% |
229: |-----|-----|-----|-----|-----|
230: | BSCANE2 | 0 | 0 | 4 | 0.00 |
231: | CAPTUREE2 | 0 | 0 | 1 | 0.00 |
232: | DNA_PORT | 0 | 0 | 1 | 0.00 |
233: | EFUSE_USR | 0 | 0 | 1 | 0.00 |
234: | FRAME_ECCE2 | 0 | 0 | 1 | 0.00 |
235: | ICAPE2 | 0 | 0 | 2 | 0.00 |
236: | PCIE_2_1 | 0 | 0 | 1 | 0.00 |
237: | STARTUPE2 | 0 | 0 | 1 | 0.00 |
238: | XADC | 0 | 0 | 1 | 0.00 |
239: |-----|-----|-----|-----|-----|
240:

```

Figure 2.8 (Utilization report part5)

Figure 2.9 (Utilization report part5)

TIMING REPORT

A Timing Report was also run, and as expected, the higher our module in our hierarchy or the more a module was called, the worse the timings were according to Vivado.

TOP_DAWG	84
mod1 (Clk_0)	33
mod2 (lfsr_10bit)	30
mod9 (seven_segment_controller)	20
mod0 (Clk)	1

Figure 2.10 (Timing report given)

BASYS BOARD IMPLEMENTATION

The results of our BASYS board implementation can be seen below. However the system is hard to demonstrate using images, so a video is included in the file submission on blackboard. Which will demonstrate the system working at a very fast clock speed. Looking at the photos below, we are able to see that the seven segment is displaying a number of multiple six, showing us that the BASYS is indeed counting correctly. We can also see the bits shown in different sequences on our LED while the ENGAGE switch is enabled. The last case of RESET enabled also shows a correct result of our count returning to 0.

 


Figure 2.11 (System working at fast clock)

Figure 2.11 (System working normally)

 


Figure 2.8 (Reset engaged, count rest to 0 and binary number retuned to seed)

CONCLUSION

In this lab we were able to create a Moore Machine FSM to sequentially count the occurrence of a pattern appearing. By incorporating the knowledge acquired from our past Lab and assignments. We were able to create new modules such as the FSM, reuse old modules such as the LFSR, seven seg and clock modules and implement test benches and constraints files to accurately program our FPGA Basys board with our system. The system counted that we found the pattern 10011110011 312 times before the LFSR cycle was done. This was done with six bits, so if we were to have only implemented the system using the 1st bit, we would have expected 51 occurrences of our pattern.

This Assignment showed how a Basys board could be used to implement different operations and showed us how a Finite State Machine can conduct operation using sequential states, and how states can overlap and not always have to go back to initial state.

REFERENCES

Code from Lab F both created and provided was modified and utilised in Assignment 2.

1. The seven segment display was used and altered to display a 15 bit number. The altered coded can be found below.

```
reg [3:0] LED_BCD;
reg [19:0] refresh_counter; // 20-bit for creating 10.5ms refresh period or 380Hz refresh rate
// the first 2 MSB bits for creating 4 LED-activating signals with 2.6ms digit period

wire [1:0] LED_activating_counter;
// count    0    -> 1 -> 2 -> 3
// activates LED1 LED2 LED3 LED4
// and repeat

always @(posedge clk or posedge reset)
begin
    if(reset==1)
        refresh_counter <= 0;
    else
        refresh_counter <= refresh_counter + 1;
end
assign LED_activating_counter = refresh_counter[19:18];
// anode activating signals for 4 LEDs, digit period of 2.6ms
// decoder to generate anode signals

always @(*)
begin
    case(LED_activating_counter)
        2'b00: begin
            anode_select = 4'b0111;
            // activate LED1 and Deactivate LED2, LED3, LED4
            LED_BCD = temp/1000;
            // the first digit of the 8-bit temperature value
        end
        2'b01: begin
            anode_select = 4'b1011;
            // activate LED2 and Deactivate LED1, LED3, LED4
            LED_BCD = (temp%1000)/100;
            // the second digit of the 8-bit temperature value
        end
        2'b10: begin
            anode_select = 4'b1101;
            // activate LED3 and Deactivate LED2, LED1, LED4
            LED_BCD = ((temp%1000)%100)/10;
            // the last digit of the 8-bit temperature value
        end
        2'b11: begin
            anode_select = 4'b1110;
            // activate LED4 and Deactivate LED2, LED3, LED1
            LED_BCD = ((temp %1000)%100)%10;
            // F symbol to indicate Fahrenheit
        end
    endcase
end
// Cathode patterns of the 7-segment LED display
always @(*)
begin
    case(LED_BCD)
        4'd0: LED_out = 7'b0000001; // "0"
        4'd1: LED_out = 7'b1001111; // "1"
        4'd2: LED_out = 7'b0010010; // "2"
        4'd3: LED_out = 7'b0000110; // "3"
        4'd4: LED_out = 7'b1001100; // "4"
        4'd5: LED_out = 7'b0100100; // "5"
        4'd6: LED_out = 7'b0100000; // "6"
        4'd7: LED_out = 7'b0001111; // "7"
        4'd8: LED_out = 7'b0000000; // "8"
        4'd9: LED_out = 7'b0000100; // "9"
        4'd10: LED_out = 7'b0111000; // "F"
        default: LED_out = 7'b0000001; // "0"
    endcase
end
endmodule
```

2. The LFSR was reused from lab F and the max_tick_reg was negated for the assignment. The code is below.

```

module lfsr_10bit
(
    input wire clk, sh_en, rst_en,
    output wire [16:0] Q_out,
    output reg fullcycle = 1'b0
);
    localparam seed = 17'h3DDF;
    reg [16:0] Q_state = 17'h0;
    wire [16:0] Q_ns;
    reg [31:0] count = 32'b0;
    wire [2:0] garbage;

    MSB_counter mod3(.clk(clk), .MSB(Q_ns[15]));

    //Clk mod1(.CCLK(clk), .clk_scale(17'd131071), .clk_tick_high, .clk_tick_low));
    //next state logic
    assign Q_fb = Q_state[16] ^ Q_state[13];
    assign Q_ns = {Q_state[15:0], Q_fb};
    //output logic

    always @ (posedge clk) begin

        if (rst_en)begin
            Q_state <= seed;
            count <= 32'b0;
        end
        else if (sh_en) begin
            count <= count + 1;
            Q_state <= Q_ns;
            if (count >= 131071)begin
                count <= 32'b0;
                fullcycle <= 1'b1;
            end
            else begin
                fullcycle <= 1'b0;
            end
        end
        else begin
            Q_state <= Q_state;
        end

        assign Q_out = Q_state;

    end

endmodule

```

3. The clock file can be also seen below, this was not changed from Lab F.

```

module Clk(
    input CCLK,
    input [31:0] clk_scale,
    output reg clk
);
    reg [31:0] clk_g = 0;

    always@(posedge CCLK)
    begin
        clk_g = clk_g + 1;

        if (clk_g >= clk_scale)
        begin
            clk = ~clk;
            clk_g = 0;
        end
    end

endmodule

```

4. The test bench was slightly modified from Lab F to test our top bench.

```

`timescale 1 ns/10 ps

module lsfr_test();
    // declaring our wires for input and output
    localparam T = 20;
    reg clk, sh_en, rst_en;
    wire [16:0] Q;
    wire tick;
    wire [9:0] count;
    //wire [16:0] tick_high, tick_low;

    // initialising our test variables with variables for display
    TOP_DAWG uut(.CCLK(clk), .RESET(rst_en), .ENGAGE(sh_en), .LED(Q));

    always
    begin
        clk = 1'b1;
        #(T/2);
        clk = 1'b0;
        #(T/2);

    end

    initial
    begin
        rst_en = 1'b1;
        #(T*10);
        rst_en = 1'b0;

    end

    initial
    begin
        sh_en = 1'b0;
        #(T*10);
        sh_en = 1'b1;
        #(T);

    end

endmodule

```